



**THE AMERICAN
UNIVERSITY IN CAIRO**

**Digital Design II
Project I
Stick Diagrams
&
Estimated Cell Height**

Mohamed A. Abdel Hamed


Fadi A. Dawoud

Eslam A. Soliman


Dr. Mohamed Shalan

Stick Diagrams:


I Tri state Inverter

 


II. Inverter

 


III. 2-input NAND

 

IV. 2-input NOR

 

 V. The Complex Function $f(x, y, z, w) = \overline{xy} + \overline{wz}$



Estimated Cell Height

By inspection of the five required cells and their sizes, the largest cell in height should be the inverter gate of size 8 since it has the tallest pull-up and pull-down networks:

$$pMOS\ network = 8 * K_p * \text{minimum } nMOS\ width$$

$$= 8 * 2.4 * 4\lambda = 76.8\lambda$$

$$nMOS\ network = 8 * \text{minimum } nMOS\ width$$

$$= 8 * 4\lambda = 32\lambda$$

Note that the above calculations do not include the needed spacing.

After doing the Layout of the x8 inverter while keeping spacing to the minimum, the cell height was **151 λ**